

Fundamental of digital systems

Arthur Herbette
Prof. Mirjana Stojilovic

Mercredi 26 mars 2025

Table des matières

1	Numbser Systems	7
1.1	Digital representations	7
1.1.1	Representation of nonnegative integers	7
	Representation of signed Integers	9
1.2	Addition of unsigned Integers	10
1.2.1	Substraction of Unsigned Integers	11
1.2.2	Two's Complement Addition/substraction	11
1.2.3	Binary multiplication	12
1.3	Fractional number	14
1.3.1	Fixed-Point Representation	14
1.3.2	Radix point	15
1.4	Concepts of finite precision math	17
1.4.1	Accuracy	17
1.4.2	Floating-Point Number representation	18
1.4.3	Significand : Sign-and-Magnitude	19
1.5	Exponent	20
	Summary	21
1.6	Rounding	21
1.6.1	IEE Standard 754	22
1.6.2	Arithmetic operations	24
	Fixed Point arithmetic Multiplication	25
	Floating-Point Arithmetic	26
1.6.3	Floating Point +/-	27
1.6.4	Not in the course	28
1.6.5	Point arithmetic	29
1.7	Digital circuit	30
1.7.1	Boolean algebra	31
1.7.2	The Venn Diagram	33
1.7.3	Logic synthesis	33
1.7.4	NANS and NOR logic Networks	36
1.7.5	Incomplety defined Functions	37
1.7.6	Adders	39
1.7.7	Fast Adders	44
1.7.8	Shifting	46
1.8	Computer Aided Design	47
1.8.1	Verilog	49
1.8.2	Tri-State Drivers	51
1.8.3	Behavioral Modeling	54

1.9 Transistors 57

Liste des cours

Cours 1 : Number Systems — Lundi 17 février 2025	5
Cours 2 : Arithmetic Operations with integers — Jeudi 20 février 2025	10
Cours 3 : Fractional (Nointeger) Number — Lundi 24 février 2025	14
Cours 4 : Arithmetic operation — Vendredi 28 février 2025	24
Cours 5 : Low precision Compute — Lundi 3 mars 2025	28
Cours 6 : Introduction to logic circuits — Jeudi 6 mars 2025	30
Cours 7 : Logic Synthesis — Lundi 10 mars 2025	33
Cours 8 : Arithmetic circuit — Vendredi 14 mars 2025	39
Cours 9 : Logisim — Lundi 17 mars 2025	47
Cours 10 : intro to CAD and Verilog — Jeudi 20 mars 2025	47
Cours 11 : tri-state drivers — Lundi 24 mars 2025	51

Juste a little test

Lundi 17 février 2025 — **Cours 1 : Number Systems**

Chapitre 1

Number Systems

1.1 Digital representations

Introduction

- In mathematics, a **tuple** is a finite ordered sequence of elements.
 - An **n-tuple** is a tuple of n elements, where n is a nonnegative integer
- In a **digital representation**, a number is represented by an **ordered n-tuple**
 - Each element of the n-tuple is called a **digit**
 - The n-tuple is called a **digit vector** (or string of digits)
 - The number of digits n is called the **precision** of the representation

1.1.1 Representation of nonnegative integers

Integer Digit-Vector

- **Digit-vector (string)** representing the integer x is denoted by :

$$X = (X_{n-1}, X_{n-2}, \dots, X_1, \overbrace{X_0}^{\text{zero-origin}})$$

We see here that it is a leftward-increasing indexing

- **Least-significant** digit (also called low order digit) : X_0
- **Most-significant** digit (also called high-order digit) : X_{n-1}

Elements of a number System

$$X = (X_{n-1}, X_{n-2}, \dots, X_1, X_0)$$

- The number system to represent the integer x consists of
 - the number of **digits** n
 - A set of numerical **values** for the digits
 - if a **set of values for a digit** X_i is D_i , the cardinality of D_i is $|D_i|$
 - A rule of interpretation
 - Mapping between the set of digit-vector values and the set of integers
 - **Set size**
 - The set of integers is a finite set of at most K elements

$$K = \prod_{i=0}^{n-1} |D_i|$$

Example : Decimal number system

$$X = (X_{n-1}, X_{n-2}, \dots, X_1, X_0)$$

(Non)Redundant Number systems

Weighted (Positional number systems

- Number of digits n
 - Can be any, but let us consider $n = 6$ (e.g., 17, 9899, 676799, ...)
 - Leading zeros are irrelevant
- Digit set in decimal number system
 - $D_i = \{0, 1, 2, \dots, 9\}$ of cardinality 10
- The corresponding set size of K is one million values, from 0 to $K - 1$
 - $K = \prod_{i=0}^{n-1} 10 = 10^6$
- A number system is **nonredundant** if
 - ... each digit-vector represents a **different** integer
 - E.g., the decimal system is nonredundant as every number is unique
- Alternatively, a number system is **redundant** if ...
 - ... there are integers represented by **more than one** digit-vector
- Most frequently used number systems are **weighted systems**
- The rule of representation :

$$x = \sum_{i=0}^{n-1} X_i W_i$$

Where $W = (W_{n-1}, W_{n-2}, \dots, W_1, W_0)$ is the **weight-vector** of size n

- Equivalent formulation :

$$x = X_{n-1}W_{n-1} + X_{n-2}W_{n-2} + \dots + X_1W_1 + X_0W_0$$

Example Decimal Number system

- Weights are a power of 10. Example :
 - Digit Vector $X = (8, 5, 4, 6, 0, 3)$
 - Weight vector $W = (10^5, 10^4, 10^3, 10^2, 10^1, 10^0)$

$$x = 8 \cdot 10^5 + 5 \cdot 10^4 + 4 \cdot 10^3 + 6 \cdot 10^2 + 0 \cdot 10^1 + 3 \cdot 10^0$$

$$x = 854703_{10}$$

- When weights are of the format
 - $W_0 = 1$ and
 - $W_i = W_{i-1}R_{i-1}, \quad i \leq i \leq n - 1$

We have a **radix number system**

Radix number system

Définition 1 *Radix number systems are weighted number system in which the weight vector is related to the **radix vector** $R = (R_{n-1}, R_{n-2}, \dots, R_1, R_0)$ as follows :*

$$W_0 = 1; \quad W_i = W_{i-1}R_{i-1}, \quad 1 \leq i \leq n - 1$$

- Equivalent to

$$W_0 = 1; \quad W_i = \prod_{j=0}^{i-1} R_j$$

	<ul style="list-style-type: none"> E.g., in the decimal number system $W_0 = 1; W_i = \prod_{j=0}^{i-1} 10$
Fixed and Mixed-Radix number systems	<ul style="list-style-type: none"> In a fixed-radix system, all elements of the radic-vector have the same value r (the radix) The weight vector in a fixed-radix system : $W = (r^{n-1}, r^{n-2}, \dots, r^2, r^1, 1)$ <p>and the integer x becomes</p> $x = \sum_{i=0}^{n-1} X_i \cdot r^i$
Example	<ul style="list-style-type: none"> Characteristics of the decimal number system : <ul style="list-style-type: none"> Radix $r = 10$ Fixed-radix system

Binary/Octal/-Hexadecimal to/from Decimal

I won't really go into the details here but the main thing to know is to convert from a system to one another (with the most famous ones)

Representation of signed Integers

Sign-and-Magnitude (SM)

- A signed integer x is represented by a pair

$$(x_s, x_m)$$


where x_s is the **sign** and x_m is the **magnitude** (positive integer)

- Sign (positive, negative) is represented by a binary variables
 - $0 \implies$ positive ; $1 \implies$ negative
- Magnitude can be represented as any positive integer
 - In a conventional radix-r system, the range of n-digit magnitude is :

$$0 \leq x_m \leq r^n - 1$$

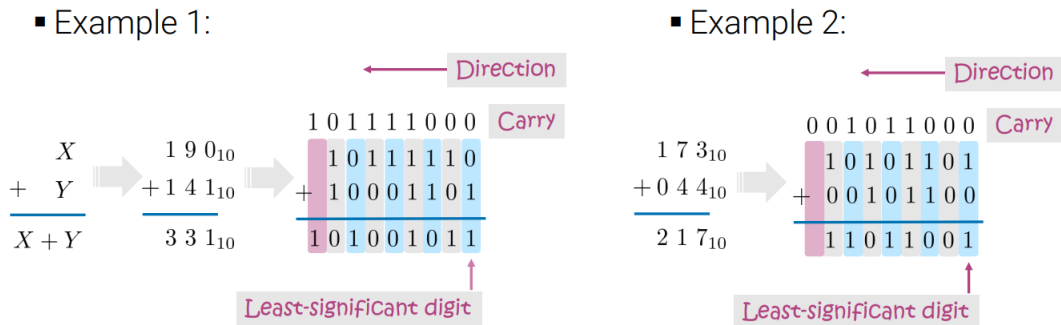1.2 Addition of unsigned Integers

By hand We use here the same principle as a classical addition by hand of decimal numbers :



CS-173, © EPFL, Spring 2025

18

How many Bits are needed To represent the **sum of two n -bit unsigned numbers** we use **$n + 1$** . For example the minimum space is when there are $0 + 0$ which leads to :

$$s_{min} = 0 + 0 = 0$$

and for the maximum :

$$s_{max} = (2^n - 1) + (2^n - 1) = 2 \cdot 2^n - 2 = 2^{n+1} - 2$$


which makes it $n + 1$ bits for the sum.

- But we do not always have the extra bit in hardware
- When the magnitude of the result exceeds the largest representable value, we say an **overflow** occurs and the result is incorrect.


1.2.1 Subtraction of Unsigned Integers

- We use here the same idea as for decimal numbers :

▪ Example 1:

 

▪ Example 2:

 

CS-173, © EPFL, Spring 2025

20

Negative result

- Negative results cannot be represented using an unsigned system
- When trying to represent a value smaller than the minimum representable by the given number of bits n , an integer **underflow** occurs, and the result is incorrect.

1.2.2 Two's Complement Addition/subtraction

Addition

We use here the same algorithm as for the unsigned numbers, and if the result exceeds the range, **overflow** occurs.

To refresh how signed numbers work, for example $1000_2 = -8_{10}$ which is the "most negative" number with 4 bits. Then we add the right side of the number as positive integers like this :


$$\underbrace{1}_{-8_{10}} \overbrace{010_2}^2 = -6_{10}$$

If we want to sum up -5 and 7 for example :

$$\begin{array}{r} 1011 + 0111 \\ \hline \overbrace{1+1}^1 0 \\ \overbrace{1}^1 10 \\ \overbrace{1}^1 010 \\ \hline 0010 = 2_{10} \end{array}$$

We use it as a clock :

 - Clockwise—addition of positive numbers
- Counterclockwise—subtraction of positive numbers



The preferred representation in digital Systems

- If we start with the smallest (most negative) number $1000_2 = -8_{10}$ and count up all successive numbers up to $0111_2 = 7_{10}$ can be obtained by adding 1 to the previous one :
 - The result will always be correct as long as the range is not exceeded
 - Simple operation
 - Not as simple for sign and magnitude
 - Good for hardware implementation
 - **Win-win** : the same hardware can perform the addition of unsigned numbers

Overflow Detection rules

- Same algorithm as for the unsigned numbers
- If the result exceeds the range, **overflow** occurs
- **Overflow detection rules**
 - If the signs of the two numbers are the same but different from the sign of the sum, the overflow occurred
 - Alternative formulation : if c_{in} into c_{out} out of the sign position are different, the overflow occurred
 - Adding two numbers of different signs never produces an overflow

1.2.3 Binary multiplication

How

We use the same "*algorithm*" that the one we use by hand. For a binary representation :

$$\begin{aligned}
 X \cdot Y &= X \cdot \sum_{i=0}^{n-1} Y_i \cdot 2^i \\
 &= \sum_{i=0}^{n-1} X \cdot Y_i \cdot 2^i \\
 &= Y_{n-1} \cdot \underbrace{X \cdot 2^{n-1}}_{\text{Mult Left-shifted by } n-1} + \dots + Y_2 \underbrace{X \cdot 2^2}_{\text{Mult Left shifted by 2}} + Y_1 \cdot X \cdot 2^1 + Y_0 \cdot X \cdot 2^0
 \end{aligned}$$

How many bits

Théorème 1 Given a n -bits integer and a m -bits integer, their product can at most require $n + m$ bits.

We can see the multiplication as a sequence of m additions with an n -bit number.

Two's Complement multiplication

Recall of a value in two's complement (signed byte) :

$$x = -X_{n-1}2^{n-1} + \sum_{i=0}^{n-2} X_i 2^i$$

- Inspired by the previous algorithm :

$$\begin{aligned} X \cdot Y &= X \cdot (-Y_{n-1} \cdot 2^{n-1}) + X \sum_{i=0}^{n-2} Y_i \cdot 2^i \\ &= -X \cdot Y_{n-1} \cdot 2^{n-1} + \sum_{i=0}^{n-2} X \cdot Y_i \cdot 2^i \\ &= -Y_{n-1} \cdot X \cdot 2^{n-1} + Y_{n-2} \cdot X \cdot 2^{n-2} + \dots + Y_2 \cdot X \cdot 2^2 + Y_1 \cdot X \cdot 2^1 + Y_0 \cdot X \cdot 2^0 \end{aligned}$$

Let us not forget the sign-extend the partial result

For this only $n + m$ bits are kept ; any higher-order bits are discarded. (that the "reason" how $-5 \cdot -3 = 15$)

I just want to underline the difference between those two representations.

Sign-Magnitude and Two's Complement

Sign Magnitude

In the Sign magnitude representation with n bits, we use the **most significant bit** (MSB) to use it as a sign :

- 0 for positive numbers
- 1 for negative numbers

The remaining bits represent the absolute magnitude of the number :

To write 5 in a 4-bits number, we use $0101_2 = +5_{10}$

To write -5 in a 4-bits number, we use $1101_2 = -5_{10}$

We see here that it is very intuitive and mirrors human notation with a sign.

Two's Complement Representation

Here, there is two point of view the one introduced in the course is to see it as a clock, in a clockwise (le sens des aiguilles d'une montre) it is positive, and unclockwise (dans le sens contraire à celui d'une montre) it is negative and begins. The negative also starts at -1 but the bit to represent -1 is 1111_2 which is just on the left.

The other way is to see it as the most significant bit (MSB) as negative, $1000_2 = -8$ and the rest of the bits being positive. To write -5 you have to write it as $-8 + 3 = -5$ which goes to $1011_2 = -5_{10}$

The pros for this notation is that there is only one representation for 0 where there is two for the other ($1000 = 0000 = 0$), The arithmetic operation are easier because we don't have to carry a sign everywhere and it is more efficient in hardware implementation.

FIGURE 1.1 – Comparison table

Feature	Sign-Magnitude	Two's complement
-5_{10}	1101	1011
Zero representation	0000(+0) and 1000(-0)	0000
Range (4-bit)	$[-7, 7]$	$[-8, +7]$

Lundi 24 février 2025 — Cours 3 : Fractional (Nointeger) Number

1.3 Fractional number

1.3.1 Fixed-Point Representation

General Format

Définition 2 *Fixed-Point Numbers are :*

- *Integers*

$$I = -N, \dots, N$$

- *Rational numbers ("binary" rationals) of the form :*

$$x = \frac{a}{2^f}$$

where $a \in I$ and f positive integer

The fixed-point representation of a number x consists of integer x_{int} and fraction x_{fr} components represented by m and f digits, respectively :

$$x = x_{int} + x_{fr}$$

Définition 3 *Digit-vector representation :*

$$X = (X_{m-1}X_{m-2} \dots X_1X_0 \underbrace{\phantom{X_{-1}X_{-2} \dots X_{-f}}}_{\text{Radix point}} X_{-1}X_{-2} \dots X_{-f})$$

- For *unsigned* numbers :

$$x = \sum_{i=-f}^{m-1} X_i 2^i$$

- For *signed* number in two's complement :

$$x = -X_{m-1}2^{m-1} + \sum_{i=-f}^{m-2} X_i 2^i$$


1.3.2 Radix point

Separator between the integer and fractional parts


$$X = (X_{m-1}X_{m-2} \dots X_1X_0 \underbrace{\phantom{X_{-1}X_{-2} \dots X_{-f}}}_{\text{Radix point}} X_{-1}X_{-2} \dots X_{-f})$$

- The position of the radix-point is assumed to be fixed
 - Hence the name fixed-point
- If the radix point is not shown, it is assumed to be to the right of the least significant digit (i.e, no fractional part)
 - In that case, the number is an integer
- Also known as decimal point, binary point, etc. . .

- No fractional part (integers)

 

- With the fractional part

 

173, © EPFL, Spring 2025

Example

- Decimal number system and $m = 5, f = 5$
- Example decimal digit vector :
 - $X = (10077.01690)$
 - $x = 1 \cdot 10^4 + 7 \cdot 10^1 \dots + 0,009$

**Fixed-point
Representation**

- Most negative (min) :

$$x_{min} = -99999.99999 = -99999 \frac{99999}{10^5}$$

- Largest number (max, positive) :

$$x_{max} = +99999.99999 = +99999 \frac{99999}{10^5}$$

- Given an unsigned fixed-point binary format $m = 3, f = 4$
— and an example binary digit vector :

$$X = (101.0111)$$

- Q : Find the equivalent decimal number :

$$X = (101.0111); x = 2^2 + 2^0 + 2^{-2} + 2^{-3} + 2^{-4} = 5.4375$$

Example

With sign-and-magnitude and $m = 5, f = 3$, Example of a binary digit vector :

$$X = (10101.110);$$

$$x = -(4 + 1 + 0.5 + 0.25) = -5.75$$

Therefore, The most negative number can be

$$x_{min} = 11111.111_2 = -15\frac{7}{8}$$

On the other hand, the largest number :

$$x_{max} = 01111.111 = 15\frac{7}{8}$$

Two's complement

With two's complement the work is the same as usual (the first digit is negative) :

$$X = (1010.1101);$$

$$x = -8 + 2 + 0.5 + 0.0625 = -5.1875$$

Here the most negative number is $x_{min} = 1000.0000_2 = -8$
and the largest one is $x_{max} = 0111.1111_2 = 7\frac{15}{16}$

1.4 Concepts of finite precision math

Precision

Définition 4 *The precision is the maximum number of non-zero bits*

For example if we have $X = (X_{m-1}X_{m-2} \dots X_1X_0.X_{-1}X_{-2} \dots X_{-f})$ then, the precision is the sum of f and m :

$$\text{Precisions}(x) = m + f$$

Resolution

Définition 5 *The resolution is the smallest possible difference between two consecutive numbers*

For example if a number as $f = 5$ (5 digits for its fractional part) then we know that the smallest possible difference between the number is $\frac{1}{2^5} = \frac{1}{32}$, for integer ($f = 0$) the resolution is $\frac{1}{2^0} = 1$.
However, in the general case :

$$\text{Resolution}(x) = 2^{-f}$$

Rang

Définition 6 *The range is the difference between the most positive and the most negative number representable.*

For example with **two's complement**

If we take, $m = 5, f = 3$, we compute $x_{max} = \sum_{i=-f}^{m-2} 2^i = 15\frac{7}{8}$, $x_{min} = -2^{m-1} = -16$. Then, the range is equal to $x_{max} - x_{min} = 31\frac{7}{8}$.
In the general case, for fixed point and two's complement :

$$\text{Range}(x) = x_{max} - x_{min} = \sum_{i=-f}^{m-2} 2^i - (-2^{m-1})$$

1.4.1 Accuracy

definition

Définition 7 *The accuracy is the magnitude of the maximum difference between a **real** value and its representation.*

The worst case (max difference) occurs for a real value exactly in the middle between two subsequent representable numbers (the real value lays between two equally distant representation).

In the general case =

$$\text{Accuracy}(x) = \frac{\text{Resolution}(x)}{2}$$

Dynamic Range

Définition 8 *The dynamic range is the **ratio** of, the maximum **absolute** value representable and the minimum positive value absolute (i.e nonzero) value representable.*

If we take the two's complement, with $m = 5, f = 3$ then the maximum absolute value is $- - 2^4 = 16$. For the minimum positive value we have

$$2^{-3} = \frac{1}{8}.$$

The dynamic range is said $= \frac{x_{max}}{x_{min}} = 128$ In the general case, for fixed-point and two's complement :

$$\text{Dynamic Range}(x) = \frac{2^{m-1}}{2^{-f}} = 2^{m-1+f}$$

<i>Personal remark</i>	You can see as the <i>size</i> of all the representable value divided by 2, 128. We have here 8 bits which means that we have 2^8 possible value which goes exactly to 256.
------------------------	---

1.4.2 Floating-Point Number representation

Floating-Point (FP) Representation

As with any other number representation in a digital system, *FP* representation is encoded in a finite number of bits. It represents only a **finite subset** of the **infinite set** of real numbers.

A real number that is **exactly** represented is called a **floating-point (FP) number**. All other real number either fall out of range (overflow or underflow) or are represented by *FP* numbers that approximate their value. The process of approximation is called **roundoff** and produces a **roundoff error**.

Significand, Exponent, Base

FP representation consists of two components :

- the signed **significand** (also called **mantissa**) M^*
- the signed **exponent** E

$$x = M^* \times b^E$$

where b is a constant called the **base**

Reminds us of the usual scientific notation, base 10 :

$$+35200 = \underbrace{3.52}_{\text{Coefficient}} \cdot 10^{+4} \quad -0.099 = -9.9 \cdot \underbrace{10^{-2}}_{\text{Exponent}}$$

Benefits of Floating-Point

Consider 32 bit two's complement signed integers :

$$\text{Dynamic Range}_1(x) = \frac{x_{max}}{x_{min}} = \frac{2^{32-1}}{2^0} = 2^{31} \approx 2 \cdot 10^9$$

New, let's consider alors a 32 bit but floating-point number, with 24-significand in sign and magnitude and 8-bits exponent in two's complement.

$$\text{Dynamic Range}_2(x) = \frac{x_{max}}{x_{min}} = \frac{(2^{23} - 1) \cdot 2^{2^{(8-1)}-1}}{2^0 \cdot 2^{-2^{8-1}}} = (2^{23} - 1) \cdot 2^{255} \approx 5 \cdot 10^{83}$$

Benefit

We can see here that the dynamic range increase a lot by a factor of $\approx 10^{74}$

We can also see the benefits the resolution which also reduces of for example when taking a 32-bits with 8 fractional bits (fixed-point) and on the other side, 24 bits significand in sign and magnitude and 8 bit exponent in two's

complement. If we compute each resolutions :

$$\begin{aligned}\text{Resolution}_1(x) &= 2^{-8} = 0.00390625 \\ \text{Resolution}_2(x) &= 2^0 \cdot 2^{-2^{(8-1)}} = 2^{-2^7} = 2^{-128}\end{aligned}$$

If we compute the ratio :

$$\frac{\text{Resolution}_2(x)}{\text{Resolution}_1(x)} = \frac{2^{-128}}{2^{-8}} = 2^{-120} \approx 7.523 \cdot 10^{-37}$$

1.4.3 Significand : Sign-and-Magnitude

Floating-Point Representation Today, the most used representation for significand is sign and magnitude because it simplifies multiplication in hardware. The floating-point representation becomes :

$$x = (-1)^S \times M \times b^E$$

Where $S \in \{0, 1\}$ is the **sign** and M is the **magnitude** of the signed significant

In the rest of the lecture, we assume significand is always represented in sign-and-magnitude.

Digit vector Many digit vectors are conceivable, but we focus on the following :

$$X = (\underbrace{SE_{m-1}}_{\text{Sign}E_{m-2} \dots E_1 E_0 M_{n-1} M_{n-2} \dots M_0})$$

Where E_i is the exponent and M_i is the magnitude.

There is $(n + 1)$ bit significand in **sign and magnitude** and m bit exponent.

Redundant In the most general case, the representation :

$$x = (-1)^S \times M \times b^E$$

is redundant. Sign and magnitude is redundant, Multiple magnitude and exponent combinations can give the same number.

Example

If we take for example :

$$(1010)_2 \times 2^{-2} = 10 \times 2^{-2} = 2.5$$

$$(0101)_2 \times 2^{-1} = 5 \times 2^{-1} = 2.5$$

$$(1.01)_2 \times 2^1 = 1.25 \times 2^1 = 2.5$$

Floating-point representation is **redundant unless it is normalized!**

If we take a magnitude that is **normalized** :

$$1 \leq M < 2$$

Then :

$$1010.1000_2 = 1.0101_2 \times 2^3 = 10.5$$

$$-(0.00000011)_2 = -1.1_2 \times 2^{-7} = -0.01171875$$

Juste to be clearer, the normalized one here, is $1.0101_2 \times 2^3$ and $-1.1_2 \times 2^{-7}$.

For example let put 20_{10} normalized.

First, $20_{10} = 10100_2$, however $1 \leq M < 2$, which leads us to : $1.0100_2 \times 2^4$. The M being between 1 and 2 doesn't mean that the decimal number has a 1, ...

Hidden Bit and Fraction

As the significand is normalized, the first digit of the magnitude is **always** binary 1. If something is always the same, it can be omitted (saving precious bits)

The first digit of the significand is omitted and called **hidden bit**.

The binary point is assumed to the right of the hidden bit. The represented part of the significand is called **fraction F**.

Example

$$\overbrace{101.001_2}^{\text{unnormalized significand}} \times 2^{-4} = \underbrace{1.01001_2}_{\text{Normalized significand}} \times 2^{-2} = \overbrace{.01001_2}^{\text{hidden is not represented}} \times 2^{-2}$$

Summary

- Common significand representation is the following :
 - Sign-and-magnitude
 - Normalized
 - One hidden bit
- Corresponding significand value becomes :

$$(-1)^S \times \left(1 + \sum_{i=1}^n M_{n-i} 2^{-i}\right)$$

1.5 Exponent

Exponent

Exponent needs to be signed

- **Positive** for representing very large numbers (**large absolute** value)
- **Negative** for representing very small numbers (**small absolute** value)

Biased representation

Exponent can take any signed representation we know but there is one particular representation, called **biased**, which simplifies comparing two *FP* numbers in hardware.

Biased representation of a digit vector $X = (X_{n-1} \dots X_1 X_0)$

$$x = \sum_{i=0}^{n-1} X_i 2^i - B$$

	Typically, the bias equals $B = 2^{n-1} - 1$
Biased re-presentation, Cntd.	Where's the catch ? <ul style="list-style-type: none"> • Resulting number are sorted just like unsigned integers but cover both the positive and negative numbers • efficient hardware (superior to two's complement) • Min exponent is represented as all zeros <ul style="list-style-type: none"> — <i>FP</i> zero can be represented as all zeros (significand and exponent)

Summary

Exponent	<ul style="list-style-type: none"> • Common representation of an $-m$ bit exponent is biased with base $B = 2^{m-1} - 1$ • For the binary digit vector :
-----------------	--

$$X = (SE_{m-1}E_{m-2} \dots E_1E_0.M_{n-1}M_{n-2} \dots M_0)$$

this biased exponent **value** becomes :

$$e = \sum_{j=0}^{m-1} E_j 2^j - (2^{m-1} - 1)$$

Floating point format	<p>There could be many floating point formats, but we will often assume :</p> <ul style="list-style-type: none"> • $(n + 1)$-bit significand • Sign and magnitude • Normalized, one hidden bit • m-bit exponent <ul style="list-style-type: none"> — Biased, $B = 2^{m-1} - 1$
------------------------------	---

$$X = (SE_{m-1}E_{m-2} \dots E_1E_0.M_{n-1}M_{n-2} \dots M_0)$$

$$x = (-1)^S \times (1 + \sum_{i=1}^n M_{n-i} 2^{-i}) \times 2^{\sum_{j=0}^{m-1} E_j 2^j - (2^{m-1} - 1)}$$

1.6 Rounding

The result of a floating-point operation is a real number that, to be represented exactly might require a significand with an infinite number of digits.

To obtain a representation close to the exact result, we perform what is called **rounding**

Rounding modes	<p>Various rounding modes exist</p> <ul style="list-style-type: none"> • Round to nearest, to even when tie • Round towards zero (truncate) • Round towards plus or towards minus infinity
-----------------------	--

Consider the real number x_{real} and the consecutive floating-point number F_1 and F_2 such that $F_1 \leq x_{real} \leq F_2$, we round it like always (normal definition)

1.6.1 IEE Standard 754

FP format in IEEE 754

Exactly what we described

- $(n + 1)$ –bit significand
- Sign and magnitude, Normalized, one hidden bit
- m –bit exponent
 - Biased $B = 2^{m-1} - 1$

$$X = (SE_{m-1}E_{m-2} \dots E_1E_0.M_{n-1}M_{n-2} \dots M_0)$$

There is two types of formats : Basic and extended format :

Basic formats

- Sign S 1 bit
- Exponent E : 8 bits
- Fraction F : 23 bits

The default rounding mode is to the nearest, to even when there is a tie.

Double precision (64 bits)

- Sign S : 1 bit
- Exponent E : 11 bits
- Fraction F : 52 bits

How to convert fixed-point to IEEE 754

In order to do this, we need 5 steps :

1. Normalize the fixed point representation by shifting the binary point to the right of leftmost
2. The mantissa is the entire binary string after the binary point (the mantissa stores the fractional part after the leading 1 which is **implicit**).
3. Calculate the exponent bits by adding the bias of 127 to the power of 2
4. Convert exponent to unsigned binary representation
5. If the number is positive, the sign bit is zero, otherwise it is 1.

Let us see for example the number such as : $13_{10}.625$.

Firstly, we convert it to binary

$$13.625_{10} = 1101.101_2$$

Now we have to normalized the binary number :

$$1.101101 \cdot 2^3$$

So :

- Mantissa : 1.101101 (the leading 1 is **implicit** in *IEEE 754*).
- Exponent : 3 (since we moved the decimal point 3 point left)

Then we compute the biased Exponent. In *IEEE* 754, we use a bias of 127 :

$$E = 3 + 127 = 130$$

$$130_{10} = 10000010$$

We then drop the leading 1 from the 1.101101, fill the rest of the bit on the right :

$$10110100000000000000000000000000$$

Which is the mantissa. this leads finally to :

$$\begin{array}{c} \text{Exponent} \\ 1 \overbrace{10000010}^{10110100000000000000000000000000} \\ \text{Mantissa} \end{array}$$

Which in hexadecimal :

$$C16C0000$$

A cool video to understand how to convert any number to *IEEE* 754 format :

<https://www.youtube.com/watch?v=RuKkePyo9zk>

Special Values

- Floating-point **zero** : $E = 0, F = 0$
 - The sign S differentiates between positive and negative zero, Value 1.0×2^{-B} is not represented.
- Positive and negative **infinity**
 - Biased exponents all ones, $F = 0$
- **NaN** (not a number)
 - To represent results of invalid operations(for example, the square root of a negative number)
 - Sign = 0 or 1 biased exponents all ones, $F \neq 0$

Exceptions : Handling of special situa- tions

The following five exceptions set a flag (i.e " *activate an alarm*") and the computation continues.

- **Overflow**, when the rounded value is **to large** to be represented
 - Result is set to infinity
- **Underflow**, when the rounded value is to small to be represented s to small to be represented
- Division by zero
- Inexact result, when the result is not an exact floating-point number
- invalid result, When *NaN* is produce by zero
- Inexact result, when the result is not an exact floating-point number
- invalid result, When *NaN* is produced

Difference between Fixed and Floating point representation

In a fixed point representation, the "distance" between each point is fixed, on the other and When using Floating point representation, this distance isn't fixed it is **floating**. The reason for this is the definition of the floating point representation :

$$X = (SE_{m-1}E_{m-2} \dots E_1E_0M_{n-1}M_{n-2} \dots M_0)$$

$$x = (-1)^S \times M \times b^E$$

As you can see, the number can be much more precise as it goes near zero.

1.6.2 Arithmetic operations**Fixed-Point arithmetic**

Performing $+$ or $-$ on two binary numbers $x(m, f)$ and $y(m, f)$ is done **the same way** as if the operands were integers.

- Overflow can happen

Example

(Slide 11) If I forgot to put the screenshot here is the example :

$$X = 000101.110_2 = 5.75_{10}$$

$$Y = 001100.011_2 = 12.375_{10}$$

And we want to sum up these two number,

$$\begin{array}{r} 00101.110 \\ +001100.011 \\ \hline \end{array}$$

We begin at the right, $0 + 1 = 1$, $X + Y = ??????.???1$ then $1 + 1 = 10$ there for we put a 0 and carry it over, $X + X = ??????.?01$, then carry+1 + 0 = 10 same method at the next index so $X + Y = ?????0.001$ then we get the carry alone, ... and we end up with $010010.001 = 18.125$

Personal remark

It is the same way because we are always adding power of the 2 event when we are in the "fractional world" it is still power of two. We also do the same with decimal number in base 10.

Two's Complement

For the two's complement the formula is :

$$x \pm y = \left(-X_{(m_x-1)}2^{(m_x-2)} + \sum_{i=-f_x}^{m_x-2} X_i2^i \right) \pm \left(-Y_{(m_y-1)}2^{(m_y-1)} + \sum_{i=-f_y}^{m_y-2} Y_i2^i \right)$$

The largest integer-part exponent : $\max(m_x-1, m_y-1)$ Consequently $m_{x \pm y} = \max(m_x, m_y) + 1$

The smallest fractional part exponent : $\min(-f_x, -f_y)$ Consequently $f_{x \pm y} =$

$\max(f_x, f_y)$

$m_{x\pm y}$ is the number of bits for the integer component that is needed (usual addition), same thing for the $f_{x\pm y}$

Fixed Point arithmetic Multiplication

Introduction

For the multiplication on two binary numbers $x(m, f)$ and $y(m, f)$, we use the same algorithm as if the operands were integers but, the **binary point location changes**.

In two's complement :

$$x \cdot y = \left(-X_{m-1}2^{m-1} + \sum_{i=-f}^{m-2} X_i 2^i \right) \cdot \left(-Y_{m-1}2^{m-1} + \sum_{i=-f}^{m-2} Y_i 2^i \right)$$

The largest integer-part exponent $(m-1) + (m-1)$ Consequently $m_{xy} = 2m$
 The smallest fractional-part exponent : $(-f) + (-f)$ Consequently $f_{xy} = 2f$

Generalization

Multiple on two binary numbers $x(m_x, f_x)$ and $y(m_y, f_y)$

$$x \cdot y = (x_{int} + x_{fr}) \cdot (y_{int} + y_{fr})$$

In two's complement :

$$x \cdot y = \left(-X_{m_x} 2^{m_x-1} + \sum_{i=-f_x}^{m_x-2} X_i 2^i \right) \cdot \left(-Y_{m_y-1} 2^{m_y-1} + \sum_{i=-f_y}^{m_y-2} Y_i 2^i \right)$$

- $m_{xy} = m_x + m_y$
- $f_{xy} = f_x + f_y$

Example : let us take for example

Analogy with

- 9.99 $m_x = 1, f_x = 2$

Decimal numbers

- 999.9999, $m_y = 3, f_x = 4$

If we take the multiplication :

$$9989.999001 \quad m_{xy} = 1 + 3 = 4; f_{xy} = 2 + 4 = 6$$

Example

For example if we take two number with the format,

- $m_x = m_y = 3$
- $f_x = f_y = 2$

and $X = 010.11, Y = 011.01$. (screenshot slide 17)

To explain it in spoken English we do it as a loop of addition without the format (like it is integer) and then with the result, we convert it to fixed-point.

We have to be careful here to not forget to change the format ($m_{xy} = m_x + m_y \dots$).

Pros and cons of fixed Point representation

Pros

- Arithmetic operations on integers can be applied to fixed-point numbers without modifications
 - Portable : we can reuse the same integer processing hardware
 - Like with integers, arithmetic operations are performed efficiently (fast)
 - Used in image and signal processing and communication

Cons

- Complex data and algorithm analysis
 - Where to put the binary point to maximize accuracy
- There are other number formats, namely floating-point, that provide more extensive dynamic range and better precision

Floating-Point Arithmetic

Addition/Subtraction

Let x and y be represented as (S_x, M_x, E_x) and (S_y, M_y, E_y)

- The significands $M^* = (-1)^S M$ are normalized

Addition/subtraction result is z , also represented as (S_z, M_z, E_z) :

$$z = x \pm y = M_x^* \times 2^{E_x} \pm M_y^* \times 2^{E_y}$$

The significand of the result is also normalized :

$$z = M_z^* \times 2^{E_z}$$

Steps

Four main steps to compute and produce the result $+/-$

- Add/subtract significand and set exponent
The significand of the number with the **smaller** exponent has to be multiplied by two to the power of the difference between the exponents (this operation is called **alignment**) and the added/subtracted to the other significand

$$M_z^* \begin{cases} (M_x^* \pm (M_y^* \times 2^{(E_y - E_x)})) \times 2^{E_x} & \text{if } E_x \geq E_y \\ ((M_x^* \times 2^{(E_x - E_y)}) \pm M_y^*) \times 2^{E_y} & \text{if } E_x < E_y \end{cases}$$

$$E_z = \max(E_x, E_y)$$

- Normalize the result and update the exponent, if required
- Round the result, normalize, and adjust exponent, if required
- Set flags for special values, if required
- Recall Step 1 : Add/subtract significand and set exponent
- Algorithm
 - Subtract exponents $d = E_x - E_y$
 - Align significands
 - Compare the exponents of the two operands
 - shift right d positions the significand of the operand with the smallest exponent
 - Select as the exponent of the result the largest exponent

Recap

- Add/subtract signed significands and produce the sign of the result

1.6.3 Floating Point +/-

Normalization Various situations may occur

- Scenario 2 : When the effective operation is an **addition**, the significand might **overflow**. Steps to perform normalization :
 - Shift right the significand one position
 - Increment the exponent by one
- Example :

$$\begin{aligned} &1.1001111 \\ &+ 0.0110110 \\ &= 10.0000101 \end{aligned}$$

Normalization

Shift right $\gg 1$

Increment the exponent $E = E + 1$

Rounding

The intermediate result may not be representable with the given format, in this case we perform a rounding.

- Towards zero : truncate the lsb
- Towards $\pm\infty$: requires addition
- To nearest : require addition

Tie to even

The *FP* result is as close as possible to the exact value :

- Minimized roundoff error (default rounding mode in *IEEE 754*)
- Tie to even is preferred because it leads to smaller error when the result is divided by two -a frequent operation

Assuming as significand of infinite precision and radix r , round to the nearest can be obtained by **adding** $(\frac{r^{-f}}{2})$ to the infinite precision significand and keeping the resulting f fractional digits

- In case of overflow : normalization and the exponent update are needed

Max round-off Error

Rounding to nearest. f fractional digits. What is the maximum difference between the exact value and its *FP* representation ?

$$d_{max} = \frac{2^{-f}}{2} \times 2^{E_{max}}$$

1.6.4 Not in the course

Exponential Growth

AI is taking on an increasingly important role. Deep neural Networks are the most widespread.

- E.g, Large models (LLM) generate human-like content

The challenge with those LLM is their size, GPT3 has 175 **Billion** parameters. Large models mean a lot of data, many computations and a fast result.

Challenges and limitations

What are the pros and cons of formats :

32-bits or 64 bit floating-point formats :

- (-) Arithmetic units are large (many bits \implies high area, high energy)
- (-) We can put fewer units per chip (e.g, less compute power in GPU)
 - Poor arithmetic density (in number of ops/mm²)
 - Fewer units, fewer computations
- (+) The model predictions are accurate, but it takes a long time to compute them

Fixed Point or integer format :

- (+) Arithmetic units are smaller and faster ($\sim 10\times$ area savings)
- (+) Better arithmetic density and lower delays
- (-) The error due to limited dynamic range are too significant for most ML models; The accuracy of their predictions suffers

New number formats are needed : The best of both worlds

Low Precision Compute

Idea

The idea is to replace the 32 bits or 64 bit *FP* number traditionally used for machine learning with reduced precision formats derived from the floating point representation

Build new, specialized hardware to accelerate ML training (**application domain specific** hardware)

Properties of low precision compute

Advantages :

- Fit more numbers in memory (larger datasets, larger models)
- Move (read/write) more number per second
- Compute faster by using more arithmetic circuit in parallel
- Energy efficiency

Disadvantages :

- Low precision
 - limits even more the set of number can represent
 - Accumulation of rounding error
- Less accurate neural network model predictions, but acceptable

Block Floating Point Imagine a block (vector) of binary numbers in *FP*. Every vector element (every number) will have its own *S/M/E*. If the exponents in the block are not too different, we could use a single **shared exponent** per block :

- **Block-floating point**

To find which shared exponent to use in a *BFP* format, we need to find the largest exponent in the block of *FP* numbers.

We use the largest because of the addition/substraction which works fine for every one of them if we take the largest

This exponent will be the shared exponent E_{block} .

Then we find the difference $d_i = E_{block} - E_i$ between the shared and each of the other exponents E_i in the block.

We then adjust the mantissa by shifting to the right the signed mantissa of each number by d_i .

Because of these adjustments, mantissa in *BFP* cannot be normalized, therefore, there is no hidden bit either.

Block floating point is only the beginning

BFP strikes a balance between arithmetic density (fewer bits used, less silicon/chip area) and range

There are many other ideas to try,

- *FP/BFP* numbers with different exponent/mantissa sizes
- Fixed point numbers with nonstandars widths
- Industry and academia are coming up with new *AI*-targeted version of number formats.

Modern application (AI) demande innovation in computing

1.6.5 Point arithmetic

Fixed Point arithmetic Addition(substraction in two's complement)

The largest integer-part exponent $\max(m_x - 1, m_y - 1)$ consequently : $m_{x \pm y} = \max(m_x, m_y) + 1$

The smallest fractional part exponent : $\min(-f_x, -f_y)$ consequently, $f_{x \pm y} = \max(f_x, f_y)$

$$x \pm y = \left(-X_{m_x-1}2^{(m_x-1)} + \sum_{i=-f_x}^{m_x-2} X_i2^i \right) \pm \left(-Y_{m_y-1}2^{(m_y-1)} + \sum_{i=-f_y}^{m_y-2} Y_i2^i \right)$$

Multiplication (Fixed Point)

$$x \cdot y = \left(-X_{m-1}2^{m-1} + \sum_{i=-f}^{m-2} X_i2^i \right) \cdot \left(-Y_{m-1}2^{m-1} + \sum_{i=-f}^{m-2} Y_i2^i \right)$$

1.7 Digital circuit

Introduction	<p>Logic circuits is the foundations of digital systems. In smartphones, computers, control systems, digital communication devices, ...</p> <p>The smallest unit of digital information is one bit, represented as a binary value 0 and 1.</p> <p>In a binary logic circuit, the electrical signals are constrained to two discrete values.</p> <p>The key to binary circuits dominance is simplicity. In practice, the two discrete values are implemented as voltage levels (the supply voltage or the ground).</p>
Two states of a switch	<p>If controlled by an input variable x, the switch is open if $x = 0$ and closed if $x = 1$.</p>
Symbol	<p>The symbol for a switch controlled by an input variable :</p>
Analyses of a logic Network	<p>Example logic network</p> <p>The sequence of input value in the truth table visualized in the network. Any sequence can be visualized in a timing diagram.</p>
Cost of logic circuit	<p>The total cost of a logic circuit is typically defined as the total number of gates plus the total number of gates input</p> <ul style="list-style-type: none"> • Each logic gate (AND, OR, NOT, etc) contributes to the cost • More inputs to gates often mean larger, more costly gates • in simplified cost models, weights may be assigned to different types of gates, depending on their complexity or physical implementation.
Functionally Equivalent Networks	<p>A logic function can be implemented with a variety of different logic networks of different cost :</p> $f(x) = \overline{x_1} + x_1x_2 = \overline{x_1} + x_2 = g(x)$ <p>The above two networks are functionally equivalent</p>
How to check for Equivalence	$f(x_1, \dots, x_n) = g(x_1, \dots, x_n), \forall x_1, x_n$ <p>Two logic networks are equivalent if :</p> <ul style="list-style-type: none"> • Their truth tables are the same • There exists a sequence of algebraic manipulation to transform one logic expression to the other (these algebraic manipulations are defined as Boolean algebra) • Their Venn diagrams are the same
How to find the best equivalent network	<p>Logic function can be implement with a variety of different networks. How does one find the best (simplest, least costly)</p>

The process of finding the best equivalent logical expression describing a logic network is called **minimization**

- **Approach 1** : Apply a sequence of algebraic transformation
 - Now always obvious when to apply which transformation, tedious, impractical
- **Approach 2** : Use **Karnaugh maps** (an alternative to the truth table)
 - Simpler, but quickly becomes unmanageable by hand (up to 4 inputs acceptable)
- **Approach 3** (the winner) Automated techniques in synthesis software tools

1.7.1 Boolean algebra

A bit of history In 1849 George Boole published a scheme for the algebraic description processes involved in logical thought and reasoning. This scheme and its refinements became known as Boolean algebra

It the late 1930s, Claude Shannon showed that Boolean algebra provides an effective means of describing circuits built with switches, therefore, Boolean algebra can be used to describe logic circuits. Boolean algebra is a powerful technique for designing and analyzing logic circuits; it is the foundation for our modern digital technology,

Axioms Like any algebra, Boolean algebra is based on a set of rules derived from a small number of basic assumptions (i.e., **axioms**). Let us assume that boolean algebra involves the following axioms are true :

1. $0 \cdot 0 = 0$
 $1 + 1 = 1$
2. $1 \cdot 1 = 1$
 $0 + 0 = 0$
3. $0 \cdot 1 = 0 \cdot 1 = 0$
 $1 + 0 = 0 + 1 = 1$
4. if $x = 0$, then $\bar{x} = 1$
if $x = 1$, then $\bar{x} = 0$

From the axioms, we can define some rule (i.e., **theorems**) for dealing with single boolean variables

Single variable theorems If x is a variable, then the following theorems hold :

1. $x \cdot 0 = 0$
 $x + 1 = 1$
2. $x \cdot 1 = x$
 $x + 0 = x$
3. $x \cdot x = x$
 $x + x = x$
4. $x \cdot \bar{x} = 0$
 $x + \bar{x} = 1$
5. $\bar{\bar{x}} = x$

Theorems grouped in pairs, emphasizing the **principle of duality**.

Dual Form is obtained by replacing all $+$ operators with \cdot operators, and vice versa; and by replacing all 0s with 1s, and vice versa.

To prove the theorems, apply **perfect induction** (i.e., substitute the variable with 1 or 0) and use the axioms.

Two and three variable properties

Given three Boolean variables, the following properties hold :

- Commutative $x \cdot y = y \cdot x$
 $x + y = y + x$
- Associative : $x \cdot (y \cdot z) = (x \cdot y) \cdot z$
 $x + (y + z) = (x + y) + z$
- Distributive : $x \cdot (y + z) = x \cdot y + x \cdot z$
 $x + y \cdot z = (x + y) \cdot (x + z)$

Example

Let us prove the validity of the following logic equation :

$$(x_1 + x_3)(\overline{x_1} + \overline{x_3}) = x_1\overline{x_3} + \overline{x_1}x_3$$

Let us manipulate the left hand side :

$$\begin{aligned} (x_1 + x_3)(\overline{x_1} + \overline{x_3}) &= (x_1 + x_3)\overline{x_1} + (x_1 + x_3)\overline{x_3} \\ &= x_1\overline{x_1} + x_3\overline{x_1} + x_1\overline{x_3} + x_3\overline{x_3} \\ &= 0 + x_3\overline{x_1} + x_1\overline{x_3} + 0 \\ &= x_1\overline{x_3} + \overline{x_1}x_3 \end{aligned}$$

Purpose

The purpose of the axioms, theorems, and properties in Boolean Algebra is to perform algebraic transformation to do :

- **Check for equivalence**, Find if two logical expressions (i.e., logical circuits made of gates) are equivalent (i.e., perform the same functionality) without evaluating all input possibilities
- **Design efficient circuits** Simplify the logical expression to find a potentially more efficient equivalent variant (i.e., design a circuit of the same desires functionality but with fewer gates)

Two and three variable properties :

Given three boolean variable, the following properties hold :

- Absorption : $x + x \cdot y = x$
 $x \cdot (x + y) = x$
- Combining $x \cdot y + x \cdot \overline{y} = x$
 $(x + y) \cdot (x + \overline{y}) = x$
- DeMorgan's theorem : $\overline{x \cdot y} = \overline{x} + \overline{y}$
 $\overline{x + y} = \overline{x} \cdot \overline{y}$
- Redundancy : $x + \overline{x} \cdot y = x + y$
 $x \cdot (\overline{x} + y) = x \cdot y$
- Consensus : $x \cdot y + y \cdot z + \overline{x} \cdot z = x \cdot y + \overline{x} \cdot z$
 $(x + y) \cdot (y + z) \cdot (\overline{x} + z) = (x + y) \cdot (\overline{x} + z)$

Proof

For example let us prove the validity of the following logic equation :

$$x_1\overline{x_3} + \overline{x_2}x_3 + x_1x_3 + \overline{x_2}x_3 = \overline{x_1}x_2 + x_1x_2 + x_1\overline{x_2}$$

Use the left hand side for the manipulation :

$$\begin{aligned}
 x_1\overline{x_3} + \overline{x_2}\overline{x_3} + x_1x_3 + x_1x_2 + \overline{x_2}x_3 &= x_1\overline{x_3} + x_1x_3 + \overline{x_2}\overline{x_3} + \overline{x_2}x_3 \\
 &= x_1(\overline{x_3} + x_3) + \overline{x_2}(\overline{x_3} + x_3) \\
 &= x_1 \cdot 1 + \overline{x_2} \cdot 1 \\
 &= x_1 + \overline{x_2}
 \end{aligned}$$

1.7.2 The Venn Diagram

Introduction Venn Diagram provides a graphical illustration of various operations and relations in the algebra of sets. Popularized by John Venn (1834-1923) in the 1880s.

Shades and Contours In the diagram, the elements of a set are represented by the area enclosed by a **contour of a circle**.

- Shaded area where the **logical function** value = binary 1
- The area within the contour : **variable** value = binary 1
- The area outside the contour **variable** value = binary 0

Simple inter-section Reminder : The union of the shaded areas corresponds to the logical expression (shaded when the expression is binary 1)

Lundi 10 mars 2025 — Cours 7 : Logic Synthesis

1.7.3 Logic synthesis

Minterms For a function $f = (x_1, x_2, \dots, x_n)$ of n variables, a **product term** in which **each** of the n variables appears **once** is called a **minterm**. Minterms are typically labeled as m_i , where $i \geq 0$ is an integer. An n -variable minterm m_i can be represented by an n -bit integer.

- Variable appears **complemented** if the corresponding bit in the binary representation of m_i is 0
- Otherwise, it appears **uncomplemented** (original)

Example Let us take $n = 3, i = 5$: three variables. $5 = 101_2$ and therefore, $m_5 = x_1\overline{x_2}x_3$
 If we take now $n = 5, i = 3$: five variables. $3 = (00011)_2$ and therefore, $m_3 = \overline{x_1}\overline{x_2}\overline{x_3}x_4x_5$

Maxterms For a function $f = (x_1, x_2, \dots, x_n)$ of n variables, a **sum term** in which **each** of the n variables appears **once** is called a **maxterm**. Maxterm are typically labeled as M_i , where $i \geq 0$ is an integer. An n -variable maxterm M_i can be represented by an n -bit integer.

- Variable appears **complemented** if the corresponding **bit** in the binary representation of M_i is 1.
- Otherwise, it appears **uncomplemented** (original)

Example if we take the same as above, $n = 3, i = 5$ with $5 = 101_2$ we get :

$$M_5 = \overline{x_1} + x_2 + \overline{x_3}$$

And as we take the second way, $n = 5, i = 3$ we get :

$$x_1 + x_2 + x_3 + \overline{x_4} + \overline{x_5}$$

What we are doing here is the same thing as seen in AICC I, we use it the same way as CNF and DNF where one is with negation on the 1 and the *OR* between each variable and the other with *AND* everywhere but the opposite.

This is equivalent because of the Morgan's law.

Logic synthesis with Minterm/- Maxterms

For a function f specified in the form of a truth table, a logic expression realizing the function can be obtained by considering :

- Only the rows in the table for which $f = 1$ or
- Only the rows in the table for which $f = 0$

If we are considering the rows where $f = 1$, f is represented by the **sum of the minterms** corresponding to the rows where $f = 1$.

If we are considering the rows where $f = 0$, f is described by **the product of the maxterms** corresponding to the rows where $f = 0$

Sum of pro- ducts (SoP) form

When we are considering the rows where $f = 1$, f is represented by the sum of the corresponding minterms. The resulting logical expression is correct but **not** necessarily the lowest cost (optimal) implementation of f .

Any logical expression consisting of product (AND) terms that are summed (OR) is said to be in the **sum-of-products (SoP)** form.

Définition 9 We called the **canonical sum of products** where all the product are a minterm

Example SoP Consider a function f of $n = 3$ variables and the truth table below :


x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Then, the canonical SoP form :

$$\begin{aligned} f(x_1, x_2, x_3) &= \sum(m_1, m_4, m_5, m_6) \\ &= \sum m(1, 4, 5, 6) \end{aligned}$$

$$\begin{aligned}
 f(x_1, x_2, x_3) &= \overline{x_1}x_2x_3 + x_1\overline{x_2}x_3 + x_1x_2\overline{x_3} + x_1x_2x_3 \\
 &= \overline{x_2}x_3 + x_1x_3
 \end{aligned}$$

Which get us to :

 

A good indication of the **cost** of a logic circuit is the total number of **gates** and the **input** to the gates in the circuit.

- For the design above, the cost = 5 + 1 + 1 + 2 + 2 + 2 = 13 where 5 is the total gates, the one's are the NOT, 2's are the AND and OR.

Example PoS

Now we consider with product instead of a sum. Consider a function f of $n = 3$ variables and the truth table below :

$$\begin{aligned}
 f(x_1, x_2, x_3) &= \prod(M_0, M_2, M_3, M_7) \\
 &= \prod M(0, 2, 3, 7)
 \end{aligned}$$

$$\begin{aligned}
 f(x_1, x_2, x_3) &= M_0 \cdot M_2 \cdot M_3 \cdot M_7 \\
 &= (x_1 + x_2 + x_3)(x_1 + \overline{x_2} + x_3)(x_1 + \overline{x_2} + \overline{x_3})(\overline{x_1} + \overline{x_2} + \overline{x_3})
 \end{aligned}$$

And now using the Morgan's theorem :


$$f = \overline{\overline{f}} = \overline{m_0 + m_2 + m_3 + m_7}$$

x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Which as you can see is the same as the one before, but now we only take the line with 0 as a result.

After some trick, we finally get the result :

 
$$f(x_1, x_2, x_3) = (x_1 + x_3)(\overline{x_2} + \overline{x_3})$$



 
1.7.4 NANS and NOR logic Networks

NAND and NOR gates

NAND and NOR gates can be used to build logic circuits :


 
$$f(x_1, x_2) = \overline{x_1 \cdot x_2}$$





$$f(x_1, x_2) = \overline{x_1 + x_2}$$

NAND/NOR physical implementation is simpler (requires fewer transistor) and more efficient than AND/OR. In fact the AND and OR logic gates are implemented as NAND/NOR + not. How to do we that ?:


De Morgan's Theorem

Applied to NAND and NOR

  

NOT gate using NAND or NOR

 According to Boolean theorems, $\bar{x} = \overline{x \cdot x}$ and $\bar{x} = \overline{x + x}$ which are the NAND and the NOR :



How to implement a function

Now we try to implement the function f in the *SoP* form with *NAND*


$$f = x_2 + x_1\overline{x_3}$$

Algorithm : we start by applying double inversion and, then, the Morgan's theorem to simplify the expression.

We have :

$$\begin{aligned} f &= x_2 + x_1\overline{x_3} \\ &= \overline{\overline{x_2 + x_1\overline{x_3}}} \\ &= \overline{\overline{x_2} \cdot \overline{x_1\overline{x_3}}} \end{aligned}$$

Which gives us :

 

1.7.5 Incompletely defined Functions

Incompletely defined function

are Boolean functions where some input combinations are not specified because they don't matter (e.g., they never occur), so the function does not need to define outputs for them

- Those input combinations are called **don't care conditions**

In logic optimization, don't care conditions can be assigned function value (output) either 0 or 1, to simplify the logic circuit

Example

Imagine a lion's cage with an automated door control system including two sensors and a manual override switch. **Input** :

- **Sensor L** detects if the lion is inside (1 = inside, 0 = outside)
- **Sensor T** detects if the trainer is inside (1 = inside ; 0 = outside)
- **Override switch (S)** : The trainer can manually force the door open or closed irrespective of presence (1 = override enabled ; 0 = normal mode)

Outputs

- **Door control** 1 = open, 0 = closed.

In this case with si that when $S = 1$ then L and T doesn't matter, because the door will be open in any case.

What we are doing here is this :

$$D = \overline{L}T\overline{S} + L\overline{T}\overline{S} + \overline{L}\overline{T}S = T\overline{S} + \overline{L}\overline{T}S$$

Which have a cost of $3 + 7 = 10$

However the result is the same by switching to

$$D = T + S$$

In spoken english this is saying, the door can only be open if the switch is on or the trainer is inside and if neither of those two are true, then the door is closed. Here the cost is $1 + 2 = 3$

Even and Odd detectors


Given the function $f = \overline{x_1}x_2 + x_1\overline{x_2}$ which we called **Exclusive OR** or *XOR* writted as \oplus :

$$f = x_1 \oplus x_2$$



$$f = x_1 \oplus x_2$$

 On the other side for the *XNOR* which is defined as $f = \overline{x_1x_2} + x_1x_2$



$$f = x_1 \odot x_2$$

Number display

I skipped the previous slides (number display) because I am late but the goal was to write on a digital clock (with the 8 which as 7 lines that can be on or off) a value $(s_1, s_0)_2$ as a decimal number. To do so you have to do first a truth table depending of which line is on depending of the values, and the create a logic function from this truth table.

Data selector

It is often helpful to choose **precisely one** from several inputs. A circuit performing data selection (a **multiplexer**) has one or more **select** inputs dedicated to determining which of the remaining inputs to pass to the output. For example, a three input multiplexer (also called 2 to 2 *MUX*) :

Inputs

- One **selection** signal s
- Two data **input** x_1 and x_2

When the selection signal is $s = 0$ the output becomes $f = x_1$ otherwise, the output becomes $f = x_2$

To write this as a logical function :

$$\begin{aligned} f(s, x_1, x_2) &= \overline{s}x_1\overline{x_2} + \overline{s}x_1x_2 + s\overline{x_1}x_2 + sx_1x_2 \\ &= \overline{s}x_1(\overline{x_2} + x_2) + s(\overline{x_1} + x_1)x_2 \\ &= \overline{s}x_1 + sx_2 \end{aligned}$$

Remark

If there are n data inputs to select from, how many select signals MUX requires ?:

$$\lceil \log_2 n \rceil$$

Because if we have two data, this give only one combination, 4 data two select signal, 2^2 , with eight data inputs, three select signals (2^3 combinations) and because we cannot take lower bound for data input that are not power of 2, we have to take the ceiling.

Vendredi 14 mars 2025 — **Cours 8 : Arithmetic circuit**

1.7.6 Adders

Adders of two 1-bit binary

Let us start from the simplest binary addition of one bit. The resulting sum is at most on two bits :

- The rightmost bit is called *sum*(s)
- The leftmost bit is called *carry*(c) ; it is produced as a carry-out when being a both bits being added are logical one

The goal is to create an addition with boolean arithmetic. Let us create a truth table :

x	y	s sum	c carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

we can as seen here, use one expression when the output is 1 for the sum and another when the output is 1 for the carry :


$$s = \bar{x}y + x\bar{y} = x \oplus y$$

For the carry :

$$c = xy$$

Which gives us the digital logic circuit :

▪ Digital logic circuit

 

▪ Graphical symbol



**Addition of two
n bit binary
number**

A binary n -bit adder has two operands $0 \leq x, y \leq 2^n - 1$ and a carry in $c_{in} \in \{0, 1\}$ as inputs, and produces as outputs :

- sum $0 \leq s \leq 2^n - 1$
- Carry out $c_{out} \in \{0, 1\}$ such that :

$$x + y + c_{in} = 2^n c_{out} + s$$

The solution to the above equation is :

$$s = (x + y + c_{in}) \mod 2^n$$

Then we get for the carry :

$$c_{out} = \begin{cases} 1 & \text{if } (x + y + c_{in}) \geq 2^n \\ 0 & \text{otherwise} \end{cases} = \lfloor \frac{x + y + c_{in}}{2^n} \rfloor$$

It is **impractical** to start from the truth table for n bit addition.

**Iterative ap-
proach**

For the iterative algorithm :

- Add each pair of bits at the position $i, 0 \leq i \leq n$
- The addition at the bit position i needs to include a carry-in at the position i (i.e., carry out from the position $i - 1$); it also generates a carry-in for the position $i + 1$

The 1 bit adder reduces to a primitive module called **full-adder (FA)** with three binary inputs and two binary outputs such that :

$$x_i + y_i + c_i = 2c_{i+1} + s_i$$

Full adder :

The goal now is to build the truth table for those outputs s_i and c_{i+1} from x_i, y_i, c_i :

x_i	y_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

With the logical expression :

$$\begin{aligned}
 s_i &= \overline{x_i}\overline{y_i}c_i + \overline{x_i}y_i\overline{c_i} + x_i\overline{y_i}\overline{c_i} + x_iy_ic_i \\
 &= (x_iy_i + \overline{x_i}\overline{y_i})c_i + (\overline{c_i}y_i + x_i\overline{y_i})\overline{c_i} \\
 &= (x_i \oplus y_i)c_i + (x_i \oplus y_i)\overline{c_i} = x_i \oplus y_i \oplus c_i
 \end{aligned}$$

And for c_{i+1} :

$$\begin{aligned}
 c_{i+1} &= \overline{x_i}y_ic_i + x_i\overline{y_i}c_i + x_iy_i\overline{c_i} + x_iy_ic_i \\
 &= (\overline{x_i}y_i + x_i\overline{y_i})c_i + x_iy_i(\overline{c_i} + c_i) \\
 &= (x_i \oplus y_i)c_i + x_iy_i
 \end{aligned}$$

Here we juste sum up the ways to get 1 for s_i and c_{i+1} .

With give us :

$$c_{i+1} = x_iy_i + x_ic_i + y_ic_i$$

Example


Let us create a full-adder from a half adders :

- Half adder :

$$\begin{aligned}
 s &= \overline{x}y + x\overline{y} = x \oplus y \\
 c &= xy
 \end{aligned}$$

- Full adder :
 
$$\begin{aligned}
 s_i &= x_i \oplus y_i \oplus c_i \\
 c_{i+1} &= (x_i \oplus y_i)c_i + x_iy_i
 \end{aligned}$$



Here we see the first result with the left **HA** and then go into a xor to the other adder

Full adder


Here the logical circuit to the final logic expression :

$$s_i = x_i \oplus y_i \oplus c_i$$


$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

is :

▪ Digital logic circuit

 

With the graphical symbol

 

And the to be able to do an addition :

- Starting from the least significant digit, we add pairs of digits, progressing to the most significant digit
- Carry "ripples" through the adder stages

There will be the same schema for the subtraction juste below but I didn't put it here again to save the picture to document ratio. (but it is the slide 15)

**Substraction
of two 1 bit bi-
nary number**

Substraction generates two bits :

- **difference** (d), the result of the subtraction
- **borrow** (b), produced as a borrow out when the subtrahend is larger than minend

Subtraction of two n-bit unsigned number

it is **impractical** to start from the truth tables for n bit subtraction, if the exact same approach as the addition :

- Subtract each pair of bits at the position $i, 0 \leq i < n$
- Subtraction at the bit position i needs to include a borrow in at position i (i.e., borrow out from the position $i - 1$); it also generates a borrow in position $i + 1$

Full subtractor

from the truth table :


x_i	y_i	b_i	d_i	b_{i+1}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Which gives us :

$$\begin{aligned}
 d_i &= \overline{x_i y_i} b_i + \overline{x_i y_i} \overline{b_i} + x_i \overline{y_i} \overline{b_i} + x_i y_i b_i \\
 &= (\overline{x_i y_i} + x_i y_i) b_i + (\overline{x_i y_i} + x_i \overline{y_i}) \overline{b_i} = (\overline{x_i \oplus y_i}) b_i + (x_i \oplus y_i) \overline{b_i} \\
 &= x_i \oplus y_i \oplus b_i
 \end{aligned}$$

$$\begin{aligned}
 b_{i+1} &= \overline{x_i y_i} b_i + \overline{x_i y_i} \overline{b_i} + \overline{x_i y_i} \overline{b_i} + \overline{x_i y_i} b_i + x_i \overline{y_i} \overline{b_i} + x_i y_i b_i \\
 &= (\overline{x_i y_i} b_i + \overline{x_i y_i} \overline{b_i}) + (\overline{x_i y_i} \overline{b_i} + \overline{x_i y_i} b_i) + (\overline{x_i y_i} b_i + x_i \overline{y_i} \overline{b_i}) \\
 &= \overline{x_i} b_i + \overline{x_i} y_i + y_i b_i
 \end{aligned}$$

 With the same principle to the n bit ripple carry subtractor :



Adders-Subtractors in two's complement

Recall that subtracting two numbers in two's complement format requires using the two's complement of one operand :

$$X - Y = X + \overline{Y} + 1$$

where

- \overline{Y} is obtained by complementing every bit of Y


- Assume a control signal op determines which operation to perform ($op = 0$ is addition and $op = 1$ is subtraction)

If we now assume a control signal op determines which operation to perform then we can create the function f :

$$f(X, Y) = \begin{cases} X + Y & \text{if } op = 0 \\ X + \bar{Y} + 1, & \text{otherwise} \end{cases}$$

Which with some boolean algebraic operations :
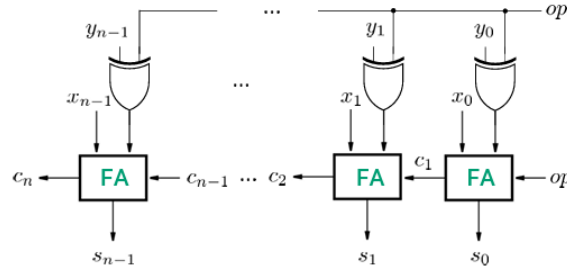
$$\begin{aligned} f(X, Y) &= \overline{op}(X + Y) + op(X + \bar{Y} + 1) \\ &= (\overline{op} + op)X + \overline{op}Y + op\bar{Y} + op \\ &= X + \overline{op}Y + op\bar{Y} + op \\ &= Xop \oplus Y + op \end{aligned}$$



1.7.7 Fast Adders

Performance Matters


Addition and subtraction are fundamental operations performed frequently. How quickly a result can be produced greatly impacts the system's performance. The performance is determined by the worst case delay. The system's value is measured as a ratio :

$$value = \frac{performance}{price}$$

Example

For example if we take the full adder :

▪ Digital logic circuit

 

with delay for each of the sum and the carry out, therefore for the worst case delay, we get :

$$\begin{aligned} t_{max} &= \max(t(s_i), t(c_{i+1})) \\ &= \max(t(XOR), t(AND) + t(OR)) \\ &= 2 \text{ Gate Delays} \end{aligned}$$

For the sum, we see that we see that every variable, x_i, y_i, c_i goes only one time into the XOR there fore :


$$\begin{aligned} t(x_i, s_i) &= t(y_i, s_i) = t(c_i, s_i) \\ &= t(XOR) \end{aligned}$$

For the carry out, if we take the path of each variable, we see that every one of them goes into a OR gate and a AND gate therefore :

$$\begin{aligned} t(x_i, c_{i+1}) &= t(y_i, c_{i+1})t(c_i, c_{i+1}) \\ &= t(AND) + t(OR) \end{aligned}$$

 Example, Input to output delay

Here we are assuming that all inputs are available at time $t = 0$:



We will do the same method as seen earlier :

- For the sum :

$$\begin{aligned} t(x_i, s_i) &= t(c_i, s_i) = t(XOR) \\ t(y_i, s_i) &= t(op, s_i) = 2t(XOR) \end{aligned}$$

- Delay to generate carry-out :

$$t(x_i, c_{i+1}) = t(c_i, c_{i+1}) = t(AND) + t(OR)$$

$$t(y_i, c_{i+1})t(op_i, c_{i+1}) = t(XOR) + t(AND) + t(OR)$$

- And then, for the worst case delay :

$$t_{max} = \max(t(s_i), t(c_{i+1}))$$

$$= \max(2t(XOR), t(XOR) + t(AND) + t(OR))$$

- And if all gates had equal delays :

$$t_{max} = t(c_{i+1}) = 3 \text{ gates delays}$$

*Basic ripple
carry adder/-
subtractor*

How can we find the **worst case delay** to find the sum/difference using a basic ripple carry adder-subtractor. We are assuming that the inputs X, Y and op are available (no waiting to start) and we are also assuming the all gates have the same delay.

The worst case delay is on the path from the op input to the last carry out output. We can find that :

$$t_{max} = t_{max}(c_1) + (n - 2)t(c_i, c_{i+1}) + t_{max}(t(c_{n-1}, c_n), t(c_{n-1}, s_{n-1}))$$

$$= t(XOR) + t(AND) + t(OR) + (n - 2)(t(AND) + t(OR)) + t(AND) +$$

Therefore if all gates are equal :

$$t_{max} = 3 + (n - 2) \cdot 2 + 2$$

$$= (2n + 1) \text{ gates delays}$$

1.7.8 Shifting

Barrel shifter

Définition 10 A **barrel shifter** is a combinational logic circuit with n data inputs n data outputs, and a set of control inputs that specify how to shift data between the input and the output

A barrel shifter inside a processor can typically specify

- **direction** of shift (left, right)
- **type** of shift (logical, arithmetic, circular/rotation)
- **amount** of shift (typically 0 to $n - 1$ bits)


implemented as a sequence of multiplexers (MUX), each shifting their input by twice as many positions as the previous MUX.

How it works


A shifting is like you could imagine with only all bits going left or right and 0 "replacing" the one that get crushed.

Shift right
by up to one
position

 - **Logical** shift resets the leading bit of the output : $l = 0$
- **Arithmetic** (sign preserving) shift : $l = x_7 = \text{Most significant bit}$



Shift right by
Up to seven
position

 

Lundi 17 mars 2025 — Cours 9 : Logisim


Jeudi 20 mars 2025 — Cours 10 : intro to CAD and Verilog

Previously on
FDS

- We implemented $+/-$ arithmetic circuits using logic gates
 - Basic building blocks : full adder and subtractor
 - N -bit ripple carry adder in two's complement
- Discovered the importance of circuit delay (Examples of critical path delay computation)
- Built fast adders : Carry-select adder
- Barrel shifters
 - Used multiplexers to perform logic arithmetic shift

 1.8 Computer Aided Design

Introduction to CAD tools Logic circuit found in today's complex computing systems cannot be designed manually, Designers of logic circuits heavily rely on the availability of **computer-aided design (CAD)** tool :



Design Entry

Design entry is the starting point in the process of designing a logic circuit. The conception of what the circuit is supposed to do and the formulation of its general organization and structure. It is performed by the designers without the guidance of CAD tools, it requires experience and intuition.

<p><i>Approach 1 : Schematic capture</i></p>	<p>The goal here is to draw the logic gates and interconnecting them with wires, schematics tools provide libraries of gates and other circuit components.</p> <ul style="list-style-type: none"> • Hierarchical design : Subcircuits previously created can be represented as graphical symbols and included (reused) in the schematic
<p><i>Approach 2 : Hardware description language</i></p>	<p>An HDL is similar to a typical computer programming language except that an HDL is used to describe hardware rather than a program to be executed on a computer</p> <p>Mainstream HDL languages supported by vendors of digital hardware technology and officially endorsed as IEEE standards :</p> <ul style="list-style-type: none"> • Verilog HDL (cs-173) and VHDL
<p><i>HDL vs. Schematic capture</i></p>	<p>HDL's supported by many companies : no need to change the design from one company to another \Rightarrow Easy portability. Design entry means writing verilog source code, the code is plain text which makes it easy to include in the documentation \Rightarrow Easy sharing and reuse.</p> <p>Similar to schematic capture, HDLs support hierarchical design</p> <p>HDL source can be combined with schematic capture (e.g., a subcircuit)</p>
<p>Functional simulation</p>	<p>A circuit described in the form of logic function can be simulated to verify that it will work as expected.</p> <p>Functional simulators assume the logic functions will be implemented with perfect gates (zero-delay model)</p> <p>For the sequence of inputs specified by the designers, the simulator evaluates the circuit outputs and produces the results (e.g., timing waveforms) to be analyzed by the designers. Most often the result of this is a time diagram.</p>
<p>Physical Design</p>	<p>Mapping a circuit described in the form of logic expression into a realization that uses logic gates or other hardware components available</p> <p>Placement Determine the absolute and relative location of the hardware components on physical chip</p> <p>Routing Determine the location and shape of the wiring connections that have to be made between the inputs and outputs of the hardware components to connect them appropriately.</p>
<p>Timing simulation</p>	<p>Real circuits cannot perform their function with zero delay</p> <p>Logic propagation delay : Logic elements need time to generate a valid output whenever there are changes in the value of their inputs</p> <p>Wire propagation delay</p>
<p>Circuit implementation</p>	<p>Having ascertained that the circuit meets all desired requirements, the circuit is ready to be implemented on an actual chip</p> <p>Option ahead</p> <ul style="list-style-type: none"> • Chip fabrication (+ highest performance - extremely expensive)

- Chip configuration (+ flexible, + affordable, - lower performance)
If a programmable hardware device is used as a baseline, the desired logic functionality can be implemented by simply reprogramming the device configuration

1.8.1 Verilog

Brief history of verilog

- HDLs were introduced in the mid 1980s as languages for describing the behavior of a logic circuit
- Verilog was invented by Phil Moorby and Prabhu
 - A propriety language owned by Gateway design automation

Modeling of digital circuits in verilog

A logic circuit is specified in the form of a **module**

Option 1 : Structural modeling Gate-level modeling : Using verilog constructs to describe the structure of the circuit in terms of **circuit elements**, such as logic gates
A larger circuit is defined by writing code that instantiates the

Structural Modeling with logic gates

In structural modeling, predefined modules that implement basic logic gates are used
Logic gate instantiation statement :

```
gate_name [instance_name] (out_port, in_port{, in_port});
```

▪ Verilog built-in gates:
(incomplete list, temporarily...)


and	xor
nand	xnor
or	buf
nor	not

Note 1: The square brackets indicate an optional field

Note 2: Braces indicate that additional entries are permitted

 Example

Recall logic gate instantiation statement :




Verilog Syntax

Names


- Must start with a letter
- Can contain any letter, number, "_"

Modules in verilog

 A circuit or subcircuit described with verilog code is a **module**. Module has a name, inputs, and outputs, referred to as its **ports**



Full adder in verilog

 

Algorithm

- Name your circuit
 - That will be the name of your verilog module
- Label all inputs and outputs
 - Those will be the input and output port names of your verilog module
- Label all logic gates
 - Those will be the names of your gates instances
 - same gate type can be instantiated multiple times, provided the instance name is unique
- Label all internal nets
 - Those will be the names of the wires in your Verilog module

Concrete code

Here is how the code of the full adder would look like :

```

// Structural modeling of a full-adder

module fulladd (a, b, c_in, s, c_out);
  // ----- port definitions -----
  input  a, b, c_in;
  output s, c_out;
  // ----- intermediate signals -----
  wire  w1, w2, w3;
  // ----- design implementation -----
  and And1 (w1, a, b);
  and And2 (w2, a, c_in);
  and And3 (w3, b, c_in);
  or  Or1  (c_out, w1, w2, w3);
  xor Xor1 (s, a, b, c_in);
endmodule

```

Subcircuits in Verilog

A verilog module can be included as a subcircuit in another module. Modules should be defined in the same source file, in any order (or the verilog compiler must be told where each module is located). **Module instantiation statement**

module_name instance_name(.port_name ([expression]){,.port_name([expression])});

Example


For example if we take the full add module created earlier and want to structure a Four-bit ripple Carry Adder, it would gives us :

Verilog

```
module adder4 (Cin, A, B, S, Cout);
// ----- port definitions -----
input Cin;
input [3:0] A, B; // 4-bit vectors
output [3:0] S; // 4-bit vector
output Cout;

// ----- intermediate signals -----
wire [3:1] C; // 3-bit vector

 // ----- design implementation -----
fulladd stage0 (.c_in(Cin), .a(A[0]), .b(B[0]), .s(S[0]), .c_out(C[1]));
fulladd stage1 (.c_in(C[1]), .a(A[1]), .b(B[1]), .s(S[1]), .c_out(C[2]));
fulladd stage2 (.c_in(C[2]), .a(A[2]), .b(B[2]), .s(S[2]), .c_out(C[3]));
fulladd stage3 (.c_in(C[3]), .a(A[3]), .b(B[3]), .s(S[3]), .c_out(Cout));
endmodule
```



Lundi 24 mars 2025 — Cours 11 : tri-state drivers

1.8.2 Tri-State Drivers

Multiple gates driving same inputs


Imagine having two logic gate wanting to drive an input of a third logic gate. The issue here is the logic gates outputs should not be directly connected.

- If one gate forces '1' while the other forces '0', a low resistance path between the power supply and the ground would be created, and the resulting current would be high. We call that situation a **short circuit**.

Solution : Insert MUXes or tri-state drivers on the conflicting signal paths.

Tris State Drivers

 A tri-state driver has a data input, an output, and an **enable** input :




The resulting output for this is :

e	w	f
0	0	Z
1	1	Z
1	0	0
1	1	1

When we have k the number of select input is defined as $\log_2(K)$, and we rounded it up because it is defined the $2^{\text{number of bit}}$ therefore if you take $2^s = K$

 Implementing
a BUS with Tri-
state Drivers



- **Only one** of the enable signals is **active** at a time so that short circuits are avoided.
- An additional circuit that controls the activation of the **enable** signals is typically present. (which is not implemented here)

Verilog Built-In Gates Here is a complete list of the built in gate :

- **bufif** is a tri-state buffer
- **notif** is a tri-state inverter

and	xor	bufif0
nand	xnor	bufif1
or	buf	notif0
nor	not	notif1

Scalar Signal Values Verilog supports one-bit signal (scalars) and each individual signal can have one of the four values :

value	Meaning
0	logic value 0
1	logic value 1
z	or Z, tri-state (high impedance)
x	or X, unknown value or don't care

Verilog support also multi-bit signal (vectors), therefore, we can specified the value of a vector by giving a constant of the form :

$$[size] ['radix] constant$$

Where *size* is the number of bits in the constant

d	decimal
b	binary
h	hexadecimal
o	octal

Constants

If the size specifies more bits than are needed to represent the given constant, then in most casesm the constant is padded with zeors.

the exceptions to this rule are when the first character of the constant is the either x or z , in which cases the padding is done using that value.

Concatenation Operator Verilog concatenation operator `{,}` allows vectos to be combined to produce a wider resulting vector :

Example

```
wire [3 : 0] upper = 4'b1100;
wire [3 : 0] lower = 4'b0011;
wire [7 : 0] combined;
```

The the result of the concatenation :

```
assign combined = {upper, lower};
                = 8'b11000011
```

Parameters parameter associate an identifier name with constant :

Example

```
parameter n = 4;
```


Nets Nets represent connections between circuit components, it doesn't store values, but transmit the signals. The wire are like a subclass of nets, the most common net types are *wire* and *tri*. A wire is used to connect an output of one logic element in a circuit to an input of another logic element

Tri

The **tri** type denotes tri-state connections;
tri nets are treated the **same way** as the **wires**; serve to enhance **readability**

1.8.3 Behavioral Modeling

 Example For instance given an input, we can label every logic gate and wrap it up into a module for instance :



6-173, 6-FDR, Spring 2006

▪ Structural (gate level) modeling

```
module my_circuit_structural (
    input x1, x2, x3, x4,           Inputs and outputs can be defined
    output f                       between the parentheses, for readability
);

    wire w1, w2, w3, w4, w5, w6, w7, w8;

    and (w1, x1, x3);
    not (w2, x2);
    not (w3, x3);
    and (w4, x2, x4);
    or (w5, x1, w3);
    or (w6, w2, x4);
    or (w7, w1, w4);
    and (w8, w5, w6);
    or (f, w7, w8);
endmodule
```

50

Behavioral modeling Gate-level modeling becomes tedious for large circuit, the alternative is to use abstract expression and programming constructs to **describe** the **behavior** of a logic circuit.

```
always @*
[begin]
[procedural assignments]
[if-else statements]
[case statements]
[while, repeat, and for loops]
[task and function calls]
[end]
```

All the operator can be use not only on the bits but on a vector.

Continuous assignments

The **assign** keyword provides a **continuous assignment for a signal**

The term continuous stems from the use of Verilog in simulation of logic circuits.

- Whenever any signal on the right hand side of the assignment changes its value, the signal on the left-hand side will be re-evaluated
- **Continuous assignments are executed in parallel** : Therefore, the order in which they appear in the code is irrelevant.

for example, if we take $f = w7 \mid w8$ whenever $w7$ or $w8$ change, f **will be re-evaluated**.

Procedural statements

We can use all the "high" level programming statements such as *if – else*, *case*, loops...

hardware. However we kind of go away from the root and the "only" logic gate . Therefore,

Procedural statements **must** be contained inside an **always**-block :

- Evaluated in the order given in the code.

To describe circuit behavior, variable are used instead of wires.

- For circuit modeling, variables of type *reg* are used

Always block

The general format if a always block is given as :

```
always @*
[begin]
[procedural assignments]
[if-else statements]
[case statements]
[while, repeat, and for loops]
[task and function calls]
[end]
```

The square brackets indicate an optional field

When multiple statements are included in the block, the begin and end keywords are needed.

always write the (arobase)*.

Full adder

For example if we wanted to created a full adder, we use a **case** statemants to describe the truth tables :

x	y	<i>Cin</i>	s	<i>Cout</i>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Which gives us the following code :

```

module fulladd (
  input x, y, Cin,
  output reg s, Cout);

  always @* begin
    case ({x, y, Cin})
      3'b000: {s, Cout} = 'b00;
      3'b001: {s, Cout} = 'b10;
      3'b010: {s, Cout} = 'b10;
      3'b011: {s, Cout} = 'b01;
      3'b100: {s, Cout} = 'b10;
      3'b101: {s, Cout} = 'b01;
      3'b110: {s, Cout} = 'b01;
      3'b111: {s, Cout} = 'b11;
    endcase
  end
endmodule

```

Verilog concatenation operator {,}
allows vectors to be combined
to produce a wider resulting vector.

40

1.9 Transistors

There is too much schema for me to juste screenshot them and put it in the pdf, so until page 16 of the pdf Lecture -Digital Logic, Part VI, implementation technology.